

F215 Digital Design — Tutorial 2

Canonical forms, K-maps, NAND/NOR universal gates, requirements-to-circuit design

Question 1: NAND/NOR-Only Implementations (Universal Gates)


A fire-alarm circuit computes $F = AB + A'C$, where A = smoke detected, B = heat detected, C = CO confirmed.

- (a) Draw a circuit for F using NOT, AND, and OR gates directly (any number of inputs per gate is fine).


A note on NAND gates

By De Morgan's law:
 
$$\overline{x \cdot y} = \bar{x} + \bar{y}$$



(a) AND-invert

 


(b) Invert-OR

This means a NAND gate can be drawn two equivalent ways: as an AND gate with a bubble on its output (NOT of AND), or as an OR gate with bubbles on both inputs (OR of inverted inputs). Both symbols compute exactly the same function — which form you draw just depends on which is easier to match against the rest of your circuit.


A note on NOT gates

 The same idea applies to a plain inverter: it can be drawn as the usual triangle-with-bubble symbol, or shorthand as just a bare bubble sitting on a wire. This is the form you'll use when bubble-pushing through a circuit — a bubble on a wire is a NOT gate.



inverter symbol

=

 


bare bubble on a wire

- (b) Using this information, convert your circuit from (a) into an all-NAND implementation: take the circuit and add bubbles at the appropriate points so every gate becomes a NAND gate. (Hint: two bubbles on a wire cancel each other because $\text{NOT}(\text{NOT}(x)) = x$). How would you implement the NOT gate needed for the A' input using only a NAND gate?

 
- (c) The CO sensor turns out to be unreliable on its own, so the design is revised to only trust a CO reading when it agrees with a high-temperature reading: $F = AB + A'BC$. Convert this to an all-2-input-NAND circuit (use as is without simplification).

A note on NOR gates

By the dual form of De Morgan's law: $\overline{x + y} = \bar{x} \cdot \bar{y}$



(a) OR-invert

 

(b) Invert-AND

So a NOR gate can also be drawn two equivalent ways: as an OR gate with a bubble on its output, or as an AND gate with bubbles on both inputs.

- (d) Now implement the original $F = AB + A'C$ using only NOR gates. Before you start bubble-pushing on the AND-OR circuit from (a), it's worth asking whether there's a different algebraic form of F that might make this a much easier task.

Question 2: Canonical Forms, Minimization, and Choosing SOP vs. POS

Table 1

G	E	J	R
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Table 2

G	E	J	R
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

- Write the canonical sum-of-products expression for R using minterms based on Table 1.
- Use a K-map to reduce this to a minimal sum of products (MSP).
- Find the minimal SOP for R using a K-map for Table 2.
- Now find the minimal POS for R using a K-map — group the 0s instead of the 1s, and use the maxterm rule to write each sum term.
- Compare the two forms from (c) and (d): how many gates does each need, and how many total gate-inputs? Which would you build, and why?

Question 3 — From Requirements to a Circuit: A Complete Design

A wireless sensor node transmits a 3-bit reading $D_2D_1D_0$ to a base station over a noisy link. To help the receiver catch single-bit transmission errors, the transmitter also sends one extra check bit P alongside the three data bits. The transmitter hardware is built so that, no matter what the 3-bit reading is, the total count of 1s among D_2 , D_1 , D_0 , and P always comes out even.

- Build the truth table for P as a function of D_2 , D_1 , D_0 .
- Derive the MSP for P. What is the gate count for implementing P? Can it be implemented with fewer gates?
- On the receiver side, how will you test if the received 4-bit value ($D_2D_1D_0P$) is correct or has exactly one bit corrupted? Design a circuit for this.
- Now we devise a different method to detect errors. The sensor encodes values in Gray code. The receiver circuit provides two outputs: the previous received value, and the current received value. Design a circuit that detects errors in the current value, under the assumption that readings change slowly, so consecutive readings can only be identical or neighbouring values.
 - For each bit position, how would you compute whether that bit changed between the previous and current reading?
 - Given those three change-signals, how many can be 1 at once for a valid transition, and how many indicates an error? Design a circuit that outputs $ERROR = 1$ exactly when too many bits changed.